

Study of Zener Diode and IC 7805

Sabarno Saha

22MS037

Grp. B-10

*Indian Institute of Science Education and Research, Kolkata,
Mohanpur, West Bengal, 741246, India.*

Contents

1	Aim	2
2	Theory	2
2.1	Zener Diode	2
2.2	IC 7805	3
3	Zener Diode	3
3.1	Line Regulation	3
3.2	Load Regulation	4
3.2.1	Approaching Breakdown Region	4
3.2.2	With R_c	5
4	IC 7805	6
4.1	Line Regulation	6
4.2	Load Regulation	7
5	Results	7
6	Sources of Error	8
7	Conclusion	8
8	Supplementary	9

1 Aim

The aim of this experiment is to study the characteristics of a Zener Diode and an IC 7805. The experiment is divided into two parts. In the first part, we study the line and load regulation using a Zener Diode. In the second part, we study the line and load regulation of an IC 7805, which is much more efficient than a Zener Diode.

- To study the line and load regulation of a Zener Diode.
- To study the line and load regulation of an IC 7805.

2 Theory

2.1 Zener Diode

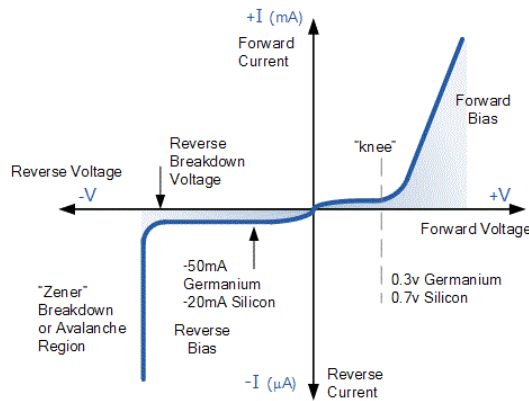


Figure 1: Typical Characteristics for a Zener Diode(Source: The Internet)

A Zener diode is a special type of diode that is designed to operate in reverse bias, unlike regular diodes which operate in forward bias. The Zener diode is designed to have a sharp increase in output current when the voltage across the diode reaches a threshold value called the breakdown voltage. The breakdown voltage is also called the Zener voltage.

When the diode is in reverse bias, there is a range where the current remains very small (in the μA range), after which the current increases sharply. This is the breakdown region. Here the voltage across the Zener diode is regulated to be constant.

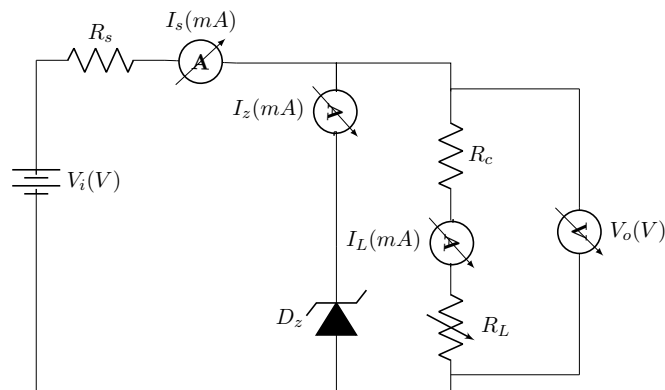


Figure 2: Circuit Diagram for Load and Line Regulation Using a Zener Diode

From the circuit diagram above, we get the following equations finding out the voltages at the nodes.

$$I_s = I_z + I_L \quad (1)$$

$$I_s = \frac{V_i - V_z}{R_s} \quad (2)$$

$$I_L = \frac{V_o}{R_c + R_L} \quad (3)$$

For our first line regulation experiment with the zener diode $R_L = 0, R_s = 2.2k\Omega, R_c = 2.2k\Omega$. Here, when we operate in the breakdown region, V_o is kept constant and V_i is varied. From here we get that

$$\delta I_s = \delta I_z \quad (4)$$

So ignoring the initial points, we should get a linear relation between I_z and I_s with slope 1, in the breakdown region. The Voltage does saturate and gets regulated in the breakdown region, but increase slowly and linearly with V_i .

For the load regulation experiment, we keep V_i constant and vary R_L . Here, we get that

$$\delta I_z = -\delta I_L \quad (5)$$

So, we should get a linear relation between I_z and I_L in the breakdown region with a slope of -1 . The voltage remains constant with the change in R_L as well.

2.2 IC 7805

Using the Zener Diode, the voltage regulation is not perfectly constant, and increases slowly and linearly with V_i . The IC 7805 is a voltage regulator that is much more efficient and much better at voltage regulation than a Zener Diode. The IC 7805 is a 3-terminal device with an input, output and a ground pin. The IC 7805, as the name suggests, regulates the output voltage to be 5V. The input pin of the of the IC 7805 is connected to the Input source Voltage and the output is connected the node where the output voltage is to be measured.

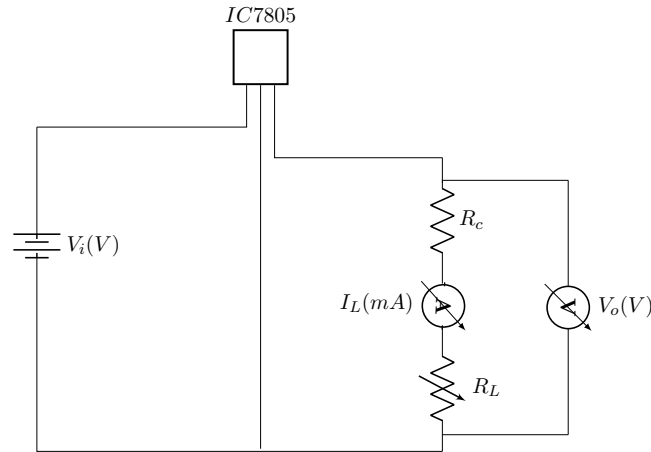


Figure 3: Circuit Diagram for Load and Line Regulation Using a IC 7805

3 Zener Diode

3.1 Line Regulation

The data for the Line regulation using a Zener Diode is given here in Table 1 in the Supplementary Section. We fix $R_s = R_c = 2.2k\Omega$ and $R_L = 0k\Omega$ and varied the input voltage. The data is plotted in the following figures. We obtain a linear fit between I_z and I_s with slope 1.002 ± 0.016 , which matches our theoretical predictions. The graph between the input and output voltage is also plotted.

From the data, we can see that the output voltage corresponding to $V_{min} = 10.51V$. The output voltage reaches almost saturation near the input voltage of $V_{min} = 10.51V$, which gives us a breakdown voltage of

$$V_b = 4.34V$$

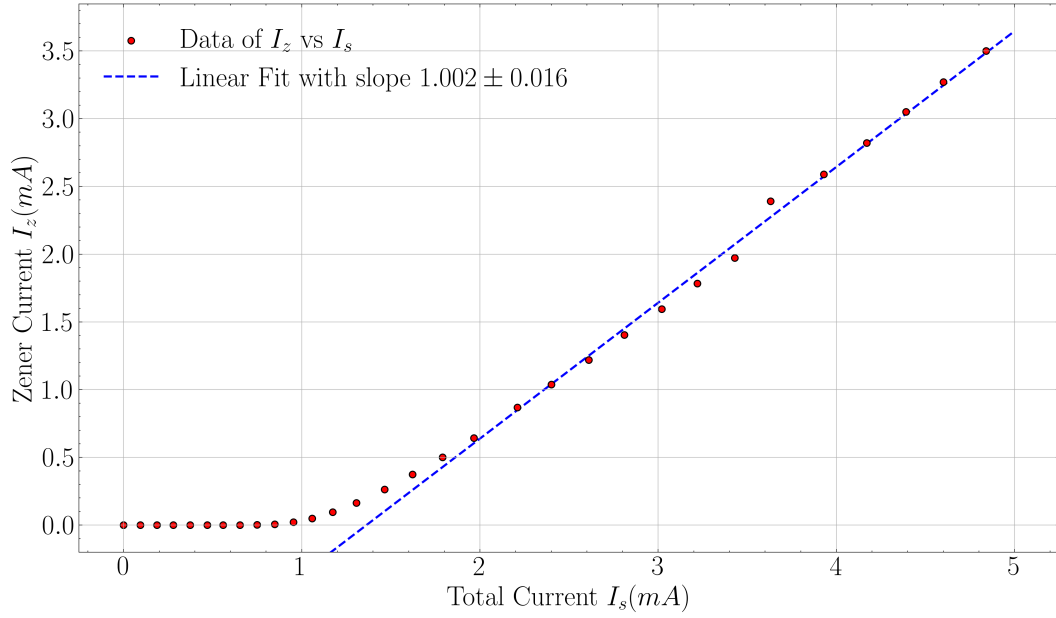


Figure 4: I_z vs I_s for Zener Diode Line Regulation

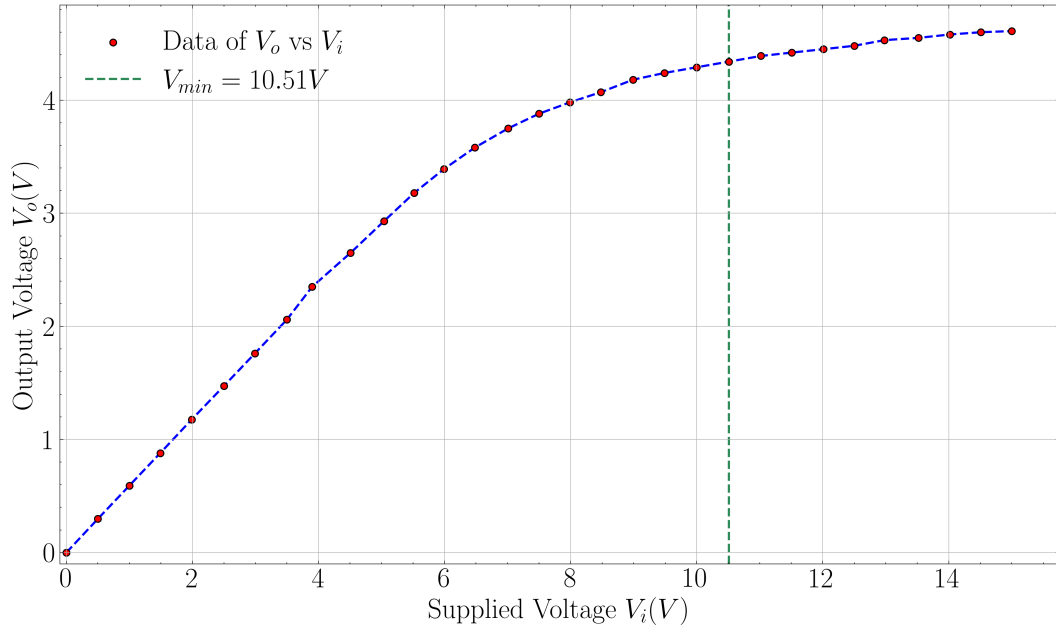


Figure 5: V_o vs V_i plot for Zener Diode Line Regulation

3.2 Load Regulation

3.2.1 Approaching Breakdown Region

The aim of this part was to see the approach to the breakdown voltage using some value of R_c that doesn't push the Zener to its breakdown region. To find out this value, we used two potentiometers one acting as R_c and the other acting as R_L . We varied the value of R_c and R_L to see the approach to the breakdown region. We then fixed the value of $R_c = 1k\Omega$ and varied the value of R_L to see the load regulation. The data is given in Table 3 in the Supplementary Section.

Note: This experiment was done on Day 2 on which we received a different Zener diode with a different breakdown voltage. The breakdown voltage was found to be around $V_b = 6.44V$, which is different from the breakdown voltage of the previous Zener Diode, used for line regulation and load regulation in the breakdown region, where $V_b \approx 4.5V$.

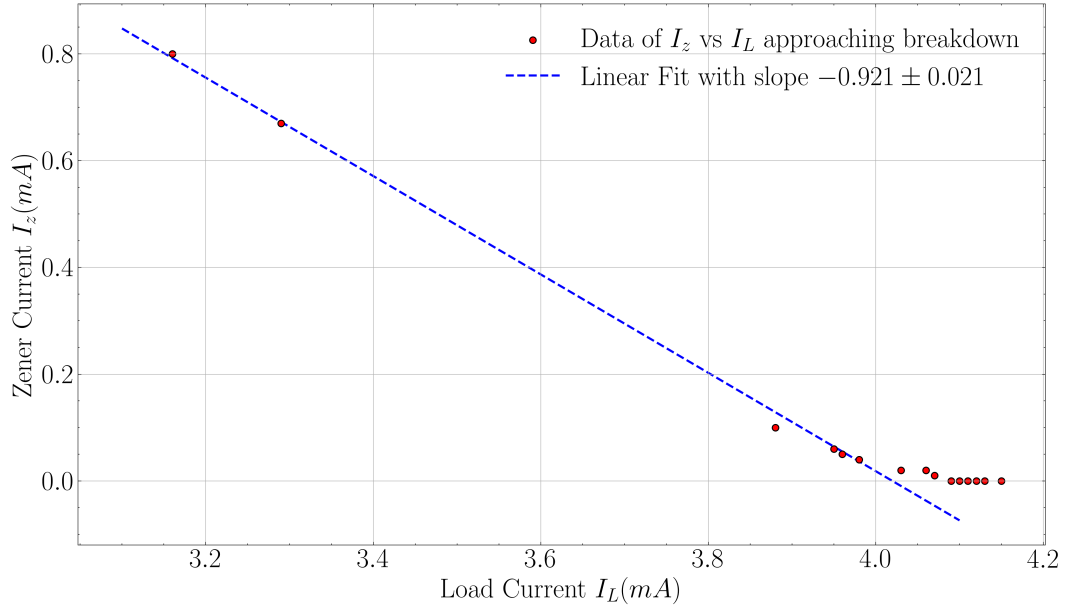


Figure 6: I_z vs I_L plot for Zener Diode Load Regulation

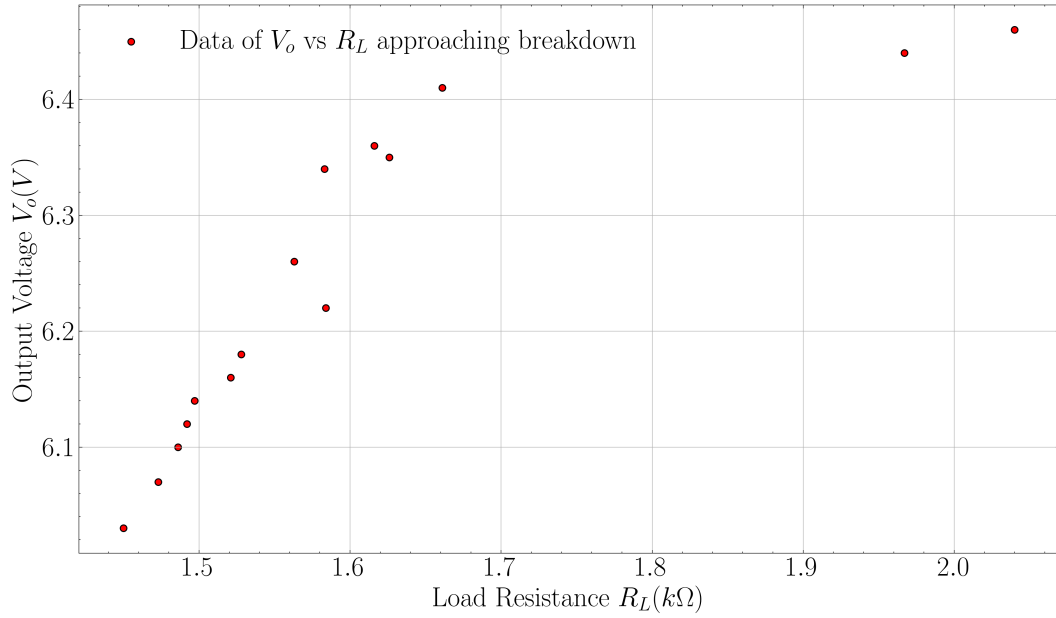


Figure 7: V_o vs R_L plot for Zener Diode Load Regulation

In the later part in the approach to the breakdown region, we get a linear relation between I_z and I_L with a slope of -0.921 ± 0.021 , which verifies $\delta I_z = -\delta I_L$.

The breakdown Voltage V_b is found out to be

$$V_b = 6.44V$$

3.2.2 With R_c

Here, for this experiment an $R_c = 2.2k\Omega$ is added so that the Zener Diode is pushed to its breakdown region. The data is given in Table 2 in the Supplementary Section.

Here again, we expect $\delta I_z = -\delta I_L$ and we get a linear relation between I_z and I_L with a slope of -0.96 ± 0.019 , which verifies out theoretical predictions.

The breakdown voltage is the average voltage over which the whole experiment takes place since, the Zener is already in its breakdown region. The breakdown voltage is found to be

$$V_b = (4.59 \pm 0.016)V$$

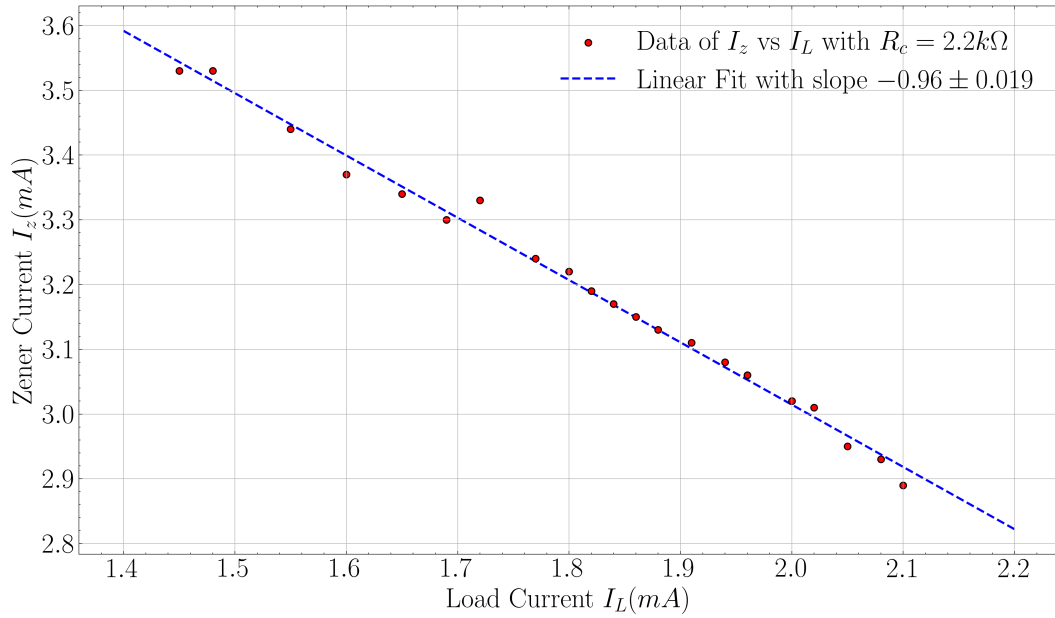


Figure 8: I_z vs I_L plot for Zener Diode Load Regulation with $R_c = 2.2k\Omega$

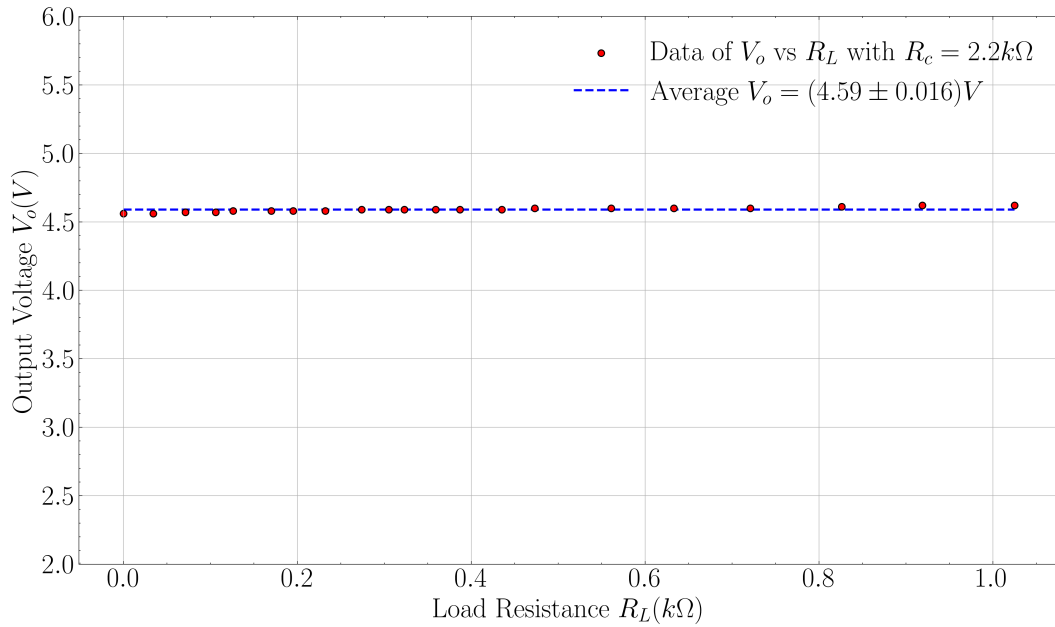


Figure 9: V_o vs R_L plot for Zener Diode Load Regulation with $R_c = 2.2k\Omega$

4 IC 7805

4.1 Line Regulation

The data for the Line regulation using an IC 7805 is given here in Table 4 in the Supplementary Section. The voltage regulation in the breakdown region for the Zener Diode is not quite constant, so we use an IC here. From the graph, it is inferred that that the input voltage reaches $V_{clamp} = 6.48$ which gives our regulated Voltage V_R as

$$V_R = 5.11V$$

The data shows that the clamping is quite efficient. It maintains the output voltage V_o to be constantly at $V_R = 5.11V$ upto the order of $10^{-2}V$, which is the resolution of our multimeter.

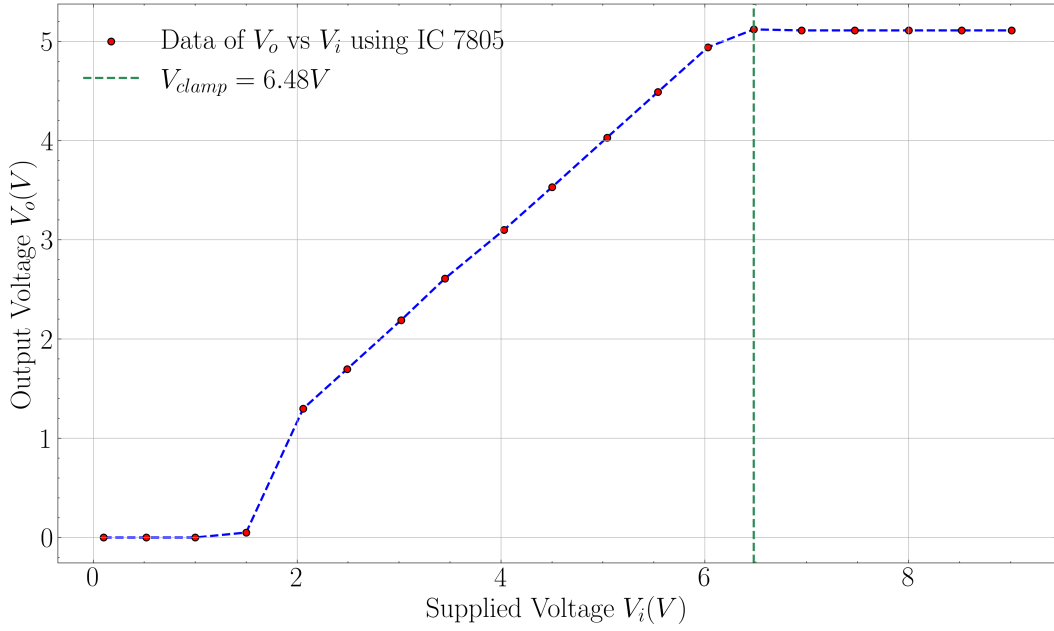


Figure 10: I_L vs V_i plot for IC 7805 Line Regulation

4.2 Load Regulation

The data for Load regulation using the IC 7805 is given in Table 5 in the Supplementary Section. For load regulation, we vary over R_L at the regulation voltage which is the average over the measured output voltages V_R ,

$$V_R = (5.022 \pm 0.012)V$$

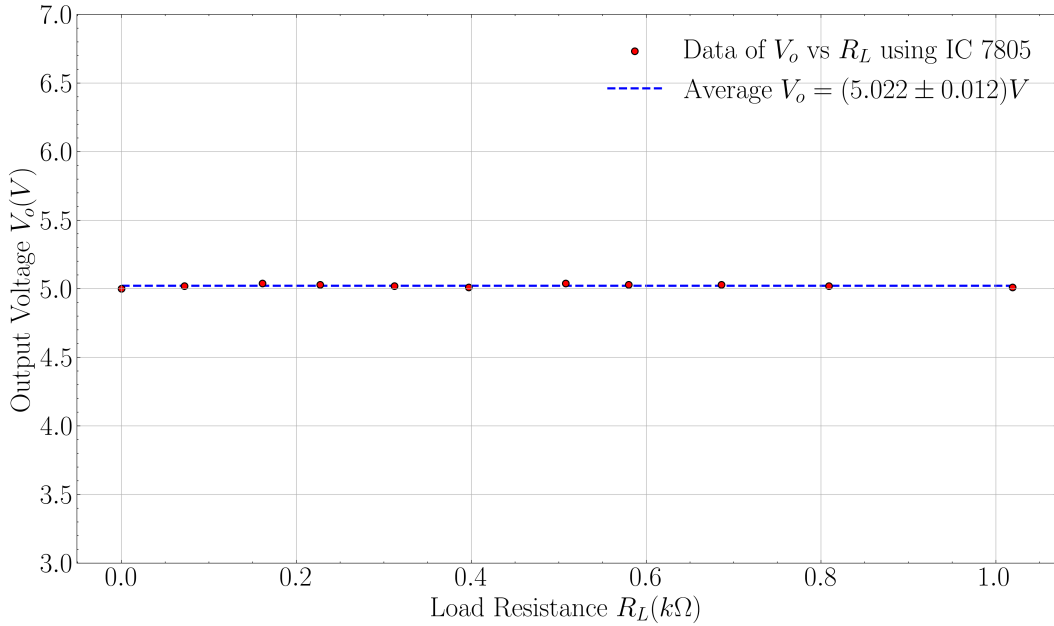


Figure 11: V_o vs R_L plot for IC 7805 Load Regulation

5 Results

We found out from this line regulation experiment with the Zener Diode that the **breakdown voltage** is $V_b = 4.34V$ when the input voltage is a minimum of $V_{min} = 10.51V$.

On Day 2, The breakdown voltage for the load regulation experiment with $R_c = 1k\Omega$ is $V_b = 6.44V$.

For the line and load regulation with IC 7805, the **regulated voltage** is $V_R = 5.11V$, which requires a minimum input voltage of $V_{clamp} = 6.48V$.

6 Sources of Error

- The multimeters have limited resolution.
- There are fluctuations in the experiment due to errors in the DC Voltage Source.
- The multimeters might have internal resistances not taken into account

7 Conclusion

We conclude the experiment by obtaining line and load regulation using the Zener Diode and then using the more efficient IC 7805.

8 Supplementary

This is a list of the tables that were obtained during the experiment.

- **Table 1:** Zener Diode Line Regulation with $R_L = 0k\Omega$
- **Table 2:** Zener Load Regulation with $R_c = 2.2k\Omega$
- **Table 3:** Zener Diode Load Regulation with $R_c = 1k\Omega$
- **Table 4:** IC 7805 Line Regulation
- **Table 5:** IC 7805 Load Regulation

V_i (V)	I_s (mA)	I_z (mA)	V_o (V)
0	0	0	0
0.5	0.094	0	0.298
1	0.187	0	0.592
1.49	0.279	0	0.88
1.99	0.373	0	1.177
2.5	0.469	0	1.473
2.99	0.559	0	1.76
3.5	0.653	0.001	2.06
3.9	0.749	0.003	2.35
4.51	0.848	0.007	2.65
5.04	0.953	0.021	2.93
5.52	1.058	0.048	3.18
5.99	1.174	0.095	3.39
6.48	1.307	0.164	3.58
7.01	1.464	0.263	3.75
7.5	1.622	0.375	3.88
7.99	1.79	0.501	3.98
8.48	1.966	0.643	4.07
8.99	2.21	0.868	4.18
9.49	2.4	1.038	4.24
10	2.61	1.218	4.29
10.51	2.81	1.403	4.34
11.02	3.02	1.595	4.39
11.51	3.22	1.784	4.42
12.01	3.43	1.972	4.45
12.5	3.63	2.39	4.48
12.98	3.93	2.59	4.53
13.52	4.17	2.82	4.55
14.02	4.39	3.05	4.58
14.51	4.6	3.27	4.6
15	4.84	3.5	4.61

Table 1: Zener Diode Line Regulation with $R_L = 0k\Omega$

$R_L(k\Omega)$	$I_L(mA)$	$I_Z(mA)$	$V_o(V)$
0	2.1	2.89	4.56
0.034	2.08	2.93	4.56
0.071	2.05	2.95	4.57
0.106	2.02	3.01	4.57
0.126	2	3.02	4.58
0.17	1.96	3.06	4.58
0.195	1.94	3.08	4.58
0.232	1.91	3.11	4.58
0.274	1.88	3.13	4.59
0.305	1.86	3.15	4.59
0.323	1.84	3.17	4.59
0.359	1.82	3.19	4.59
0.387	1.8	3.22	4.59
0.435	1.77	3.24	4.59
0.473	1.72	3.33	4.6
0.561	1.69	3.3	4.6
0.633	1.65	3.34	4.6
0.721	1.6	3.37	4.6
0.826	1.55	3.44	4.61
0.919	1.48	3.53	4.62
1.025	1.45	3.53	4.62

Table 2: Zener Load Reg. with $R_c = 2.2k\Omega$

$V_i(V)$	$I_L(mA)$	$V_o(V)$
0.1	0	0
0.52	0	0
1	0	0.0001
1.5	0.02	0.05
2.06	0.63	1.299
2.49	0.81	1.697
3.02	1.04	2.19
3.45	1.23	2.61
4.03	1.47	3.1
4.5	1.67	3.53
5.04	1.9	4.03
5.54	2.12	4.49
6.03	2.33	4.94
6.48	2.42	5.12
6.95	2.42	5.11
7.47	2.42	5.11
8	2.41	5.11
8.52	2.43	5.11
9.01	2.43	5.11

Table 4: IC 7805 Line Regulation

$R_L(k\Omega)$	$I_L(mA)$	$I_Z(mA)$	$V_o(V)$
1.45	4.15	0	6.03
1.473	4.13	0	6.07
1.486	4.12	0	6.1
1.492	4.11	0	6.12
1.497	4.1	0	6.14
1.521	4.09	0	6.16
1.528	4.07	0.01	6.18
1.584	4.06	0.02	6.22
1.563	4.03	0.02	6.26
1.583	3.98	0.04	6.34
1.626	3.96	0.05	6.35
1.616	3.95	0.06	6.36
1.661	3.88	0.1	6.41
1.967	3.29	0.67	6.44
2.04	3.16	0.8	6.46

Table 3: Zener Diode Load Regulation with $R_c = 1k\Omega$

$R_L(k\Omega)$	$V_i(V)$	$I_L(mA)$	$V_o(V)$
0	15	2.35	5
0.072	15	2.3	5.02
0.161	15	2.21	5.04
0.227	15	2.15	5.03
0.312	15	2.08	5.02
0.397	15	2	5.01
0.508	15	1.93	5.04
0.58	15	1.87	5.03
0.686	15	1.78	5.03
0.809	15	1.71	5.02
1.019	15	1.61	5.01

Table 5: IC 7805 Load Regulation